

Assembly Assignment

Mohamed Hamdan

August 2022

Problem Statement - A sequential circuit has a single input x and a single output z . The input signal x can occur in groups of 1, 2 and 3 pulses. If $x = 1$ for one clock period, the output z will be 1 for three clock periods before returning to the starting state. If $x = 1$ for two clock periods, the output z will be 1 for two clock periods before returning to the starting state. If $x = 1$ for three clock periods, the output z will be 1 for a single clock period before returning to the starting state. Construct a state diagram and implement your design with D F F s . The circuit when designed acts as a pulse width adjuster.

Hardware

Components

Component	Value	Count
Arduino	uno	1
Flip Flop	7474	2
LED	Red	1
Resistor	220ohm	1
Jumper wires	-	as required

Connections

The following connections are to be read as **IC-Name-IC-pin no:Arduino-pin no** :

- **IC7447(1)** - (1:5.5V), (2:8), (3:13), (4:5.5V), (5:2), (6:None), (7:Gnd), (8:None), (9:3), (10:5.5V), (11:13), (12:9), (13:5.5V), (14:5.5V)
- **IC7447(2)** - (1:5.5V), (2:10), (3:13), (4:5.5V), (5:4), (6:None), (7:Gnd), (8:None), (9:5), (10:5.5V), (11:13), (12:11), (13:5.5V), (14:5.5V)

Connect LED to pin 12 of arduino with the 220ohm resistor in series. Use pin 6 of arduino to input X .

State Diagram

The state diagram shown in ?? can be understood easily by grouping the states according to the clock pulse number. Consider one cycle of the state machine to contain three clock pulses numbered 1, 2 and 3. The states 0, 1 and 2 in the clock-1 group are the entry states to produce the Z values for the successive 2 clock pulses (clock-2 and clock-3). Distinct entry states are necessary in order to remember the input sequence of the previous cycle. While entering into any of these three states, the Z value for clock-1 is already determined by

the input at clock-3 of the previous cycle. In order to keep track of the number of ones in the input sequence X and to output the proper values at Z (determined by the entry state), the remaining 7 states (3-9) are required.

Since the state diagram uses 10 states, the design requires 4 DFFs. Let the present state be denoted by $\mathbf{P} = P_3P_2P_1P_0$ and the next state as $\mathbf{S} = S_3S_2S_1S_0$ with X as input and Z as output.

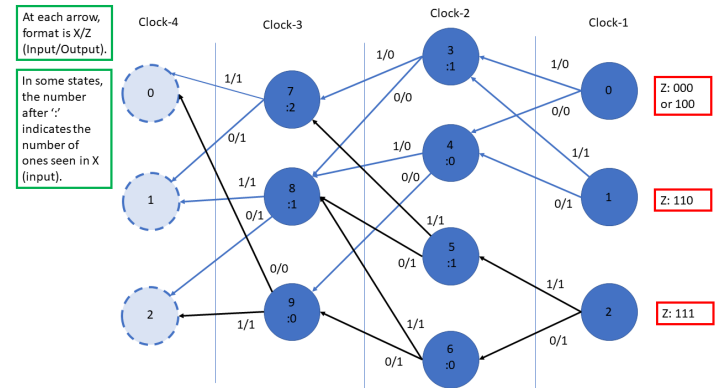


Figure 1: State diagram for pulse width adjuster

Truth table

P_3	P_2	P_1	P_0	X	S_3	S_2	S_1	S_0	Z
0	0	0	0	0	0	1	0	0	0
0	0	0	0	1	0	0	1	1	0
0	0	0	1	0	0	1	0	0	1
0	0	0	1	1	0	0	1	1	1
0	0	1	0	0	0	1	1	0	1
0	0	1	0	1	0	1	0	1	1
0	0	1	1	0	1	0	0	0	0
0	0	1	1	1	0	1	1	1	0
0	1	0	0	0	1	0	0	1	0
0	1	0	0	1	1	0	0	0	0
0	1	0	1	0	1	0	0	0	1
0	1	0	1	1	0	1	1	1	1
0	1	1	0	0	1	0	0	1	1
0	1	1	0	1	1	0	0	0	1
0	1	1	1	0	0	0	0	1	1
0	1	1	1	1	0	0	0	0	1
1	0	0	0	0	0	0	1	0	1
1	0	0	0	1	0	0	0	1	1
1	0	0	1	0	0	0	0	0	0
1	0	0	1	1	0	0	1	0	1
1	0	1	0	0	X	X	X	X	X

P_3	P_2	P_1	P_0	X	S_3	S_2	S_1	S_0	Z
1	0	1	0	1	X	X	X	X	X
1	0	1	1	0	X	X	X	X	X
1	0	1	1	1	X	X	X	X	X
1	1	0	0	0	X	X	X	X	X
1	1	0	0	1	X	X	X	X	X
1	1	0	1	0	X	X	X	X	X
1	1	0	1	1	X	X	X	X	X
1	1	1	0	0	X	X	X	X	X
1	1	1	0	1	X	X	X	X	X
1	1	1	1	0	X	X	X	X	X
1	1	1	1	1	X	X	X	X	X

Minimization using Kmap

$P_3P_2P_1 \backslash P_0X$	00	01	11	10
000	0	0	0	0
001	0	0	0	1
011	1	1	0	0
010	1	1	0	1
110	x	x	x	x
111	x	x	x	x
101	x	x	x	x
100	0	0	0	0

$P_3P_2P_1 \backslash P_0X$	00	01	11	10
000	1	0	0	1
001	1	1	1	0
011	0	0	0	0
010	0	0	1	0
110	x	x	x	x
111	x	x	x	x
101	x	x	x	x
100	0	0	0	0

$P_3P_2P_1 \backslash P_0X$	00	01	11	10
000	0	1	1	0
001	1	0	1	0
011	0	0	0	0
010	0	0	1	0
110	x	x	x	x
111	x	x	x	x
101	x	x	x	x
100	1	0	1	0

$P_3P_2P_1 \backslash P_0X$	00	01	11	10
000	0	1	1	0
001	0	1	1	0
011	1	0	0	1
010	1	0	1	0
110	x	x	x	x
111	x	x	x	x
101	x	x	x	x
100	0	1	0	0

$P_3P_2P_1 \backslash P_0X$		P_0X			
		00	01	11	10
000	0	0	1	1	
001	1	1	0	0	
011	1	1	1	1	
010	0	0	1	1	
110	x	x	x	x	
111	x	x	x	x	
101	x	x	x	x	
100	1	1	1	0	

Boolean expressions

The boolean expressions for **S** and **Z** are:

$$\begin{aligned}
 S_3 &= P_2P'_0 + P_2P'_1X' + P'_2P_1P_0X' \\
 S_2 &= P'_2P_1P'_0 + P'_2P_1X + P'_3P'_2P'_1X' + P_2P'_1P_0X \\
 S_1 &= P'_2P_0X + P'_1P_0X + P_3P'_0X' + P'_3P'_2P'_1X + P'_2P_1P'_0X' \\
 S_0 &= P'_3P'_2X + P'_2P'_0X + P_2P'_0X' + P_2P_1X' + P'_3P'_1P_0X \\
 Z &= P_1P'_0 + P_2P_0 + P_3P'_0 + P_3X + P'_3P'_1P_0
 \end{aligned}$$

Software

Make the connections and connect the arduino to the PC via USB. In the location of choice, type the below commands

1. `svn co https://github.com/Muhammed-Hamdan/iith-fwc-2022-23/trunk/fwc_arduino_asm/asm_assignment`
2. `cd ide_assignment`
3. `pio run`
4. `pio run t upload`